

AC circuit



- ✓ (i) Diode 
- ✓ (ii) Zener Diode
- ✓ (iii) Rectifier 2nd
- (iv) Transistor

32 Termin
 (1) Emitter
 (4) Base
 (11) Collector $\rightarrow V_C - V_B$
 $= V_{CB}$

BJT

PNP $\rightarrow$ X
 npn $\rightarrow$ ✓

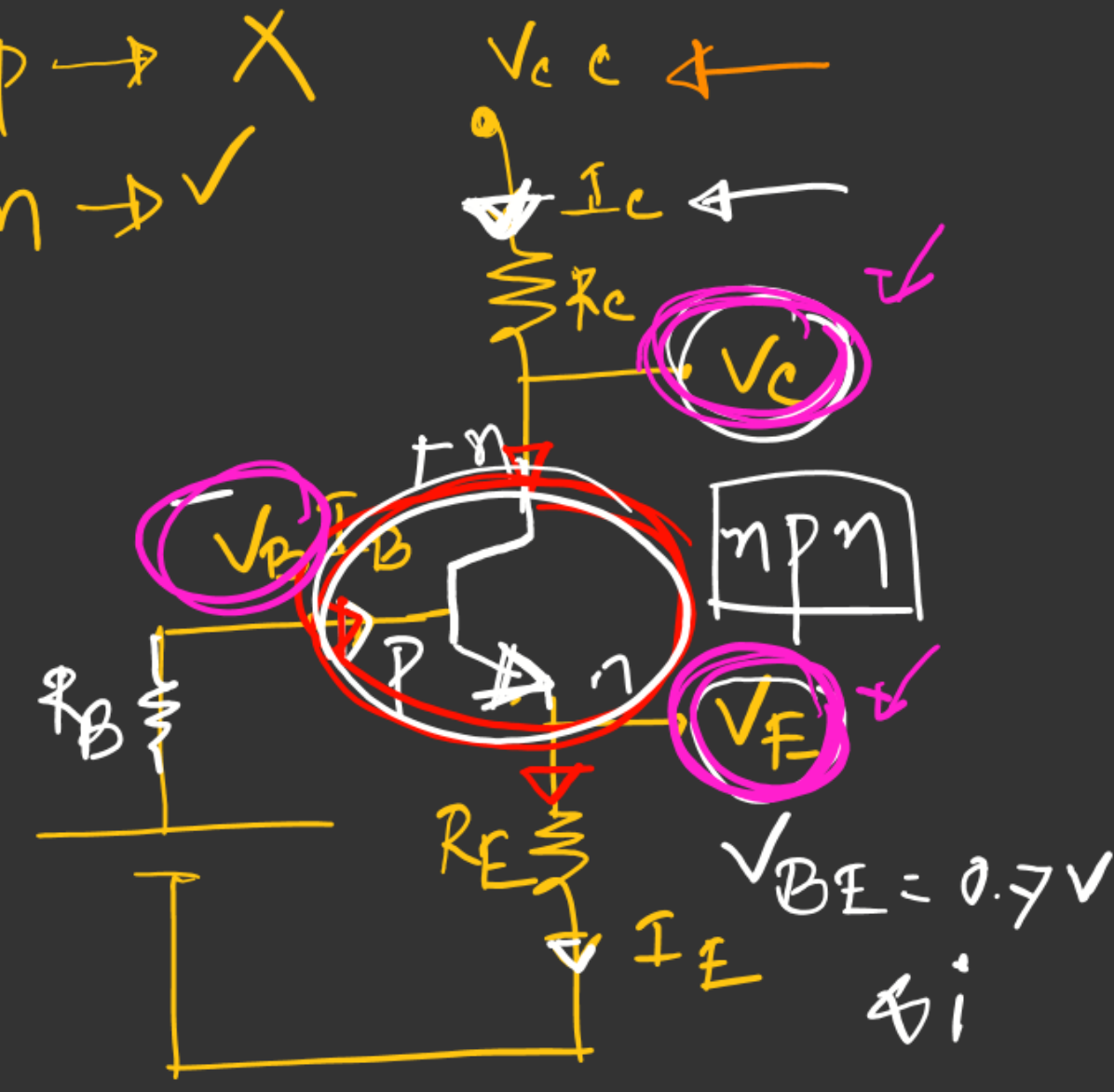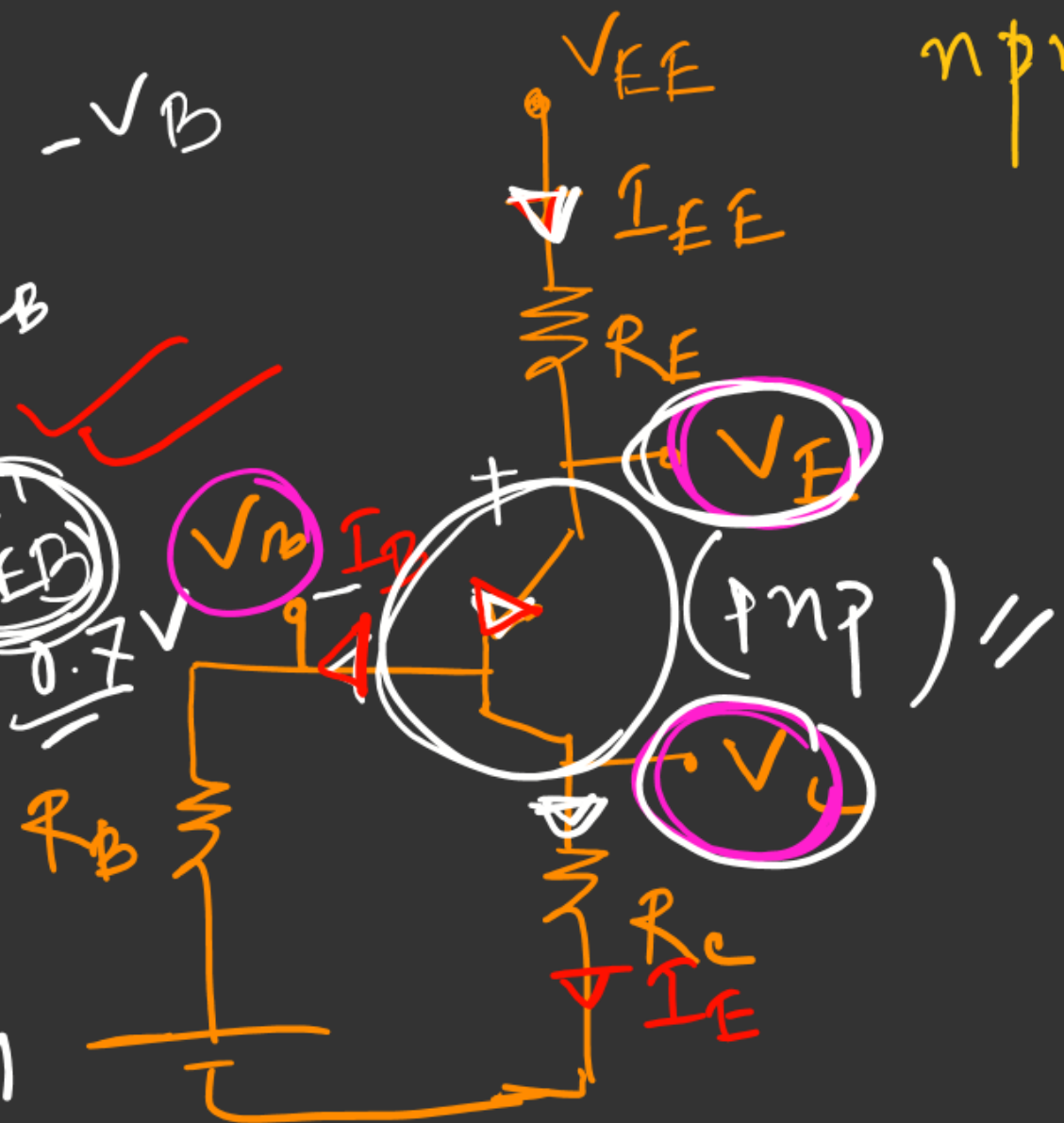$+V_E - V_B$
 $= V_{EB}$
 $= 0.7V$
 $V_{EB} = 0.7 \rightarrow$ npn
 $V_{EB} = -0.7V$



$$[I_C + I_B = I_E] \rightarrow$$

$$I_E = I_C + I_B$$

nnp/pnp

$$\textcircled{*} I_C + I_B = I_E //$$

↓

$$\beta I_B + I_B = I_E$$

$$\Rightarrow I_E = I_B(1 + \beta) //$$

* Current gain,

$$\alpha = \frac{I_C}{I_E}$$

$$\beta = \frac{I_C}{I_B} \Rightarrow I_C = \beta I_B$$

$$\gamma = \frac{I_E}{I_B}$$

$$\textcircled{*} \alpha = \frac{\beta}{\beta + 1} = \frac{\gamma - 1}{\gamma}$$

$$\textcircled{*} P = V_{CE} I_C \leftarrow \text{across}$$


* DC load line $\rightarrow$

$$I_C = 0$$

$$V_{CE}(\text{cut off}) = V_{CC}$$

$$V_{CE} = 0 \leftarrow$$
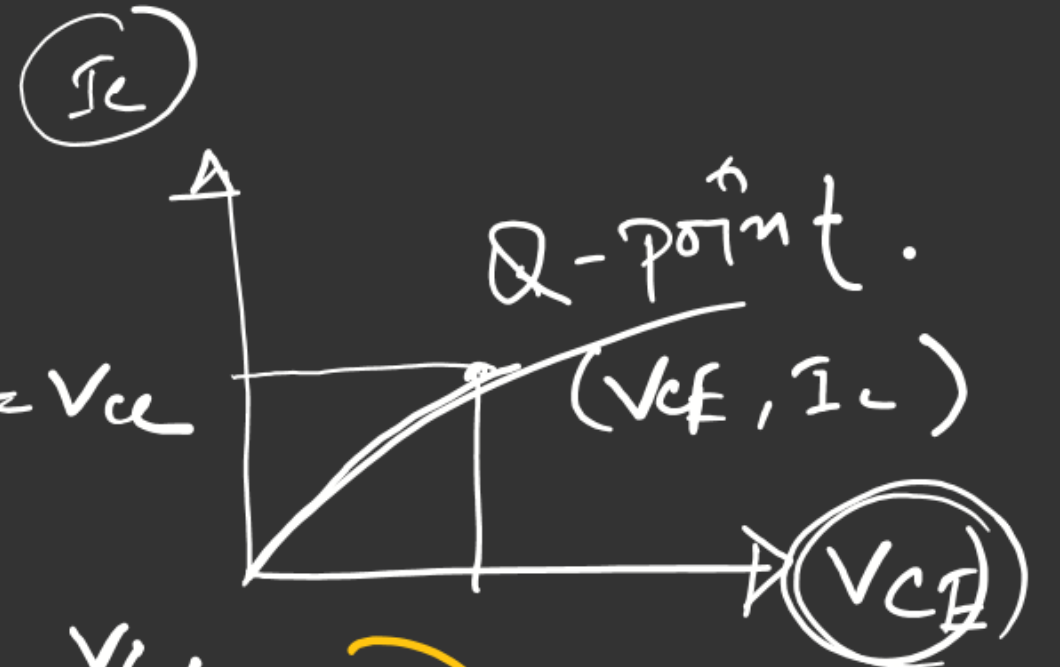
$$\left[I_C \text{ sat} = \frac{V_{CC}}{R_C + R_E} \right]$$



Transistor Mode :-

For $n p n \rightarrow$

- $V_C > V_E$ [active]
- $V_E > V_C$ [off]
- $V_C = V_E$ [saturation]

For $p n p \rightarrow$

- $V_E > V_C$ [active]
- $V_C > V_E$ [off]
- $V_E = V_C$ [saturation]

LD


$$V_{CC} - I_C R_C + V_C - V_E + V_{CE} - I_E R_E = 0$$



$$V_{CE} = I_C R_C + I_E R_E$$

$$= I_C (R_C + R_E)$$

$$I_C = \frac{V_{CC}}{R_C + R_E}$$

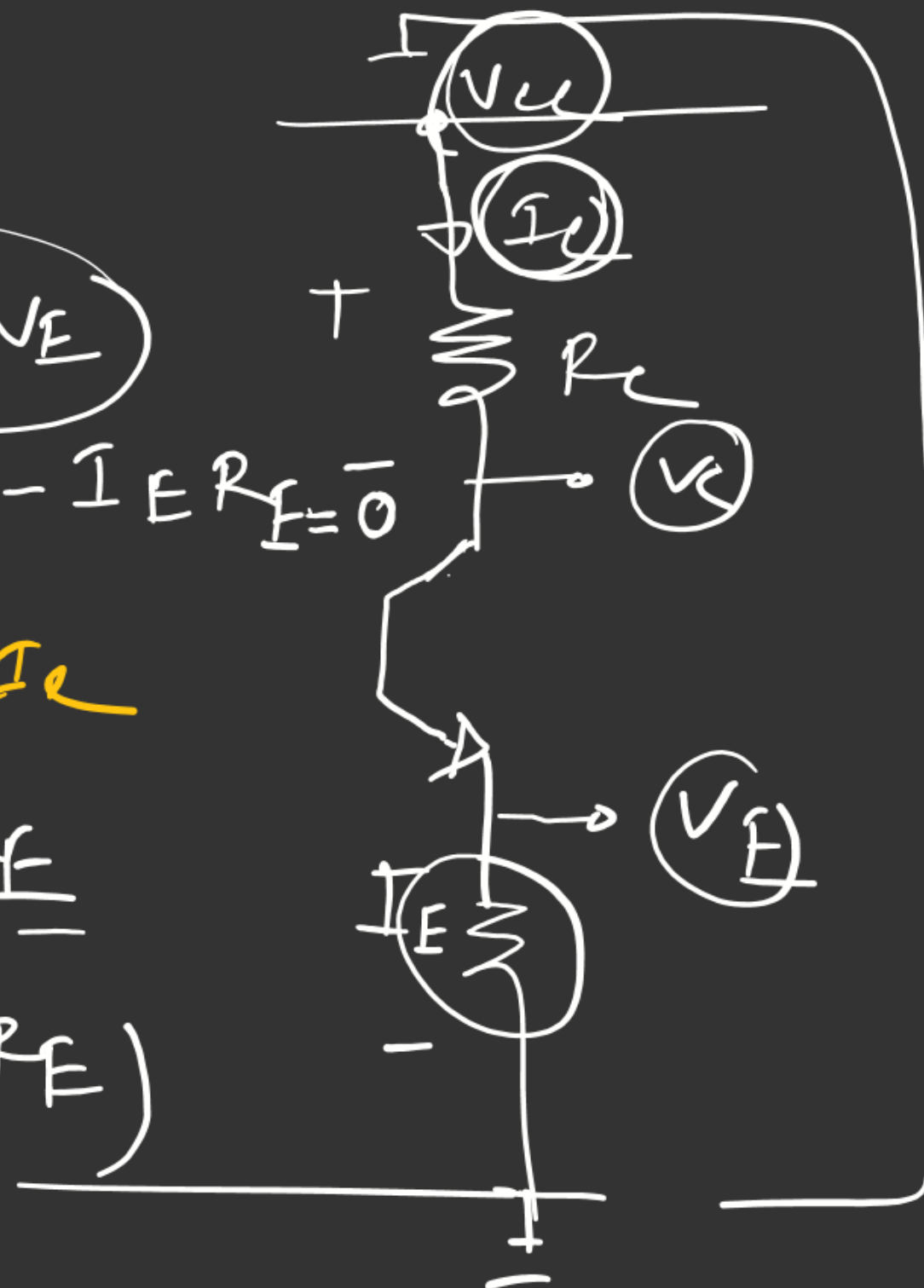

$$V_C = V_E$$

$$V_C - V_E$$

$$12 - 12 = 0$$